

ECSE 318 Lab 2 Report

Group 5

Nabeeh Daouk and Kyle Heston

Sunday, October 8, 2023

Lab Part 1_ ALU:

```
# Testing operation:      ADD=00000    //A+B=>C    signed addition
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:0014          vout:1    cout:1    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:0000000000010100    vout:1    cout:1    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:    20          vout:1    cout:1    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C:    20          vout:1    cout:1    |
#
# Testing operation:      ADDU=00001    //A+B=>C    unsigned addition
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:0014          vout:0    cout:1    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:0000000000010100    vout:0    cout:1    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:    20          vout:0    cout:1    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C:    20          vout:0    cout:1    |
#
# Testing operation:      SUB=00010    //A-B=>C    signed subtraction
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:0010          vout:0    cout:1    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:0000000000010000    vout:0    cout:1    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:    16          vout:0    cout:1    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C:    16          vout:0    cout:1    |
#
# Testing operation:      SUBU=00011    //A-B=>C    unsigned subtraction
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:0010          vout:0    cout:1    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:0000000000010000    vout:0    cout:1    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:    16          vout:0    cout:1    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C:    16          vout:0    cout:1    |
#
# Testing operation:      INC=00100    //A+1=>C    signed increment
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:8013          vout:0    cout:0    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:1000000000010011    vout:0    cout:0    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:-32749          vout:0    cout:0    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C: 32787          vout:0    cout:0    |
#
# Testing operation:      DEC=00101    //A-1=>C    signed decrement
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:8011          vout:0    cout:1    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:1000000000010001    vout:0    cout:1    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:-32751          vout:0    cout:1    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C: 32785          vout:0    cout:1    |
#
```

ALU TB: Arithmetic Operations

```
# Testing operation:      AND=01000    //A AND B
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:8002          vout:0    cout:0    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:10000000000000010    vout:0    cout:0    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:-32766          vout:0    cout:0    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C: 32770          vout:0    cout:0    |
#
# Testing operation:      OR =01001    //A OR B
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:8012          vout:0    cout:0    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:1000000000010010    vout:0    cout:0    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:-32750          vout:0    cout:0    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C: 32786          vout:0    cout:0    |
#
# Testing operation:      XOR=01010    //A XOR B
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:0010          vout:0    cout:0    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:0000000000010000    vout:0    cout:0    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C:    16          vout:0    cout:0    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C:    16          vout:0    cout:0    |
#
# Testing operation:      NOT=01100    //NOT A
# -----
# hex      INPUTS: A:8012          B:8002          CarryOutEn_L:0    |   OUTPUTS: C:7fed          vout:0    cout:0    |
# bin      INPUTS: A:1000000000010010    B:10000000000000010    CarryOutEn_L:0    |   OUTPUTS: C:0111111111101101    vout:0    cout:0    |
# dec(signed) INPUTS: A:-32750          B:-32766          CarryOutEn_L:0    |   OUTPUTS: C: 32749          vout:0    cout:0    |
# dec(unsigned) INPUTS: A: 32786          B: 32770          CarryOutEn_L:0    |   OUTPUTS: C: 32749          vout:0    cout:0    |
#
```

ALU TB: Logic Operations

```

# Testing operation:      SRL=10000 //logic left shift A by the amount of B[3:0]
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0048      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000001001000      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 72      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 72      vout:0      cout:0
#
# Testing operation:      SRL=10001 //logic right shift A by the amount of B[3:0]
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:2004      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0010000000000100      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 8196      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 8196      vout:0      cout:0
#
# Testing operation:      SLA=10010 //arithmetic left shift A by the amount of B[3:0]
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0048      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000001001000      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 72      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 72      vout:0      cout:0
#
# Testing operation:      SRA=10011 //arithmetic right shift A by the amount of B[3:0]
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:e004      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:1110000000000100      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: -8188      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 57348      vout:0      cout:0
#

```

ALU TB: Shift Operations

```

# Testing operation:      SLE=11000 //if A <= B then C(15:0) = <0...0001>
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0000      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000000000000      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 0      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 0      vout:0      cout:0
#
# Testing operation:      SLT=11001 //if A < B then C(15:0) = <0...0001>
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0000      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000000000000      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 0      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 0      vout:0      cout:0
#
# Testing operation:      SGE=11010 //if A >= B then C(15:0) = <0...0001>
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0001      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000000000001      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 1      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 1      vout:0      cout:0
#
# Testing operation:      SGT=11011 //if A > B then C(15:0) = <0...0001>
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0001      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000000000001      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 1      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 1      vout:0      cout:0
#
# Testing operation:      SEQ=11100 //if A = B then C(15:0) = <0...0001>
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0000      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000000000000      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 0      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 0      vout:0      cout:0
#
# Testing operation:      SNE=11101 //if A != B then C(15:0) = <0...0001>
# -----
# hex      INPUTS: A:8012      B:8002      CarryOutEn_L:0      | OUTPUTS: C:0001      vout:0      cout:0
# bin      INPUTS: A:1000000000010010      B:10000000000000010      CarryOutEn_L:0      | OUTPUTS: C:0000000000000001      vout:0      cout:0
# dec(signed) INPUTS: A:-32750      B:-32766      CarryOutEn_L:0      | OUTPUTS: C: 1      vout:0      cout:0
# dec(unsigned) INPUTS: A: 32786      B: 32770      CarryOutEn_L:0      | OUTPUTS: C: 1      vout:0      cout:0
#

```

ALU TB: Set Condition Operations


From Port	To Port	Max Delay	Max Process Corner	Min Delay ▼ 1	Min Process Corner
➤ B[4]	➤ C[11]	6.309	SLOW	2.620	FAST
➤ B[5]	➤ C[11]	6.320	SLOW	2.620	FAST
➤ B[6]	➤ C[11]	6.231	SLOW	2.591	FAST
➤ B[7]	➤ C[11]	6.229	SLOW	2.590	FAST
➤ A[2]	➤ C[1]	6.076	SLOW	2.587	FAST
➤ A[6]	➤ C[1]	6.076	SLOW	2.587	FAST
➤ A[10]	➤ C[1]	6.076	SLOW	2.587	FAST
➤ A[14]	➤ C[1]	6.076	SLOW	2.587	FAST
➤ B[4]	➤ C[7]	6.347	SLOW	2.584	FAST
➤ B[5]	➤ C[7]	6.369	SLOW	2.583	FAST
➤ B[4]	➤ C[15]	6.356	SLOW	2.575	FAST
➤ B[5]	➤ C[15]	6.367	SLOW	2.575	FAST

ALU Critical Path: B[4] to C[11] for behavioral addition (CLA), CLA is much faster


➤ A[2]	➤ cout	11.157	SLOW	4.641	FAST
➤ A[2]	➤ vout	11.136	SLOW	4.624	FAST
➤ A[4]	➤ cout	11.043	SLOW	4.582	FAST
➤ A[4]	➤ vout	11.023	SLOW	4.566	FAST
➤ A[1]	➤ cout	10.935	SLOW	4.528	FAST
➤ A[1]	➤ vout	10.915	SLOW	4.511	FAST
➤ A[5]	➤ cout	10.451	SLOW	4.334	FAST
➤ A[5]	➤ vout	10.431	SLOW	4.318	FAST
➤ A[0]	➤ cout	10.483	SLOW	4.302	FAST
➤ A[0]	➤ vout	10.463	SLOW	4.286	FAST
➤ B[1]	➤ cout	10.351	SLOW	4.275	FAST
➤ B[1]	➤ vout	10.331	SLOW	4.259	FAST
➤ B[0]	➤ cout	10.241	SLOW	4.205	FAST
➤ B[0]	➤ vout	10.221	SLOW	4.189	FAST
➤ B[4]	➤ C[14]	10.112	SLOW	4.163	FAST

ALU Critical Path: A[2] to cout7 for behavioral addition (ripple carry adder)


Lab Part 2_ CPU:

 

CPU: Verilog Module Level Architecture

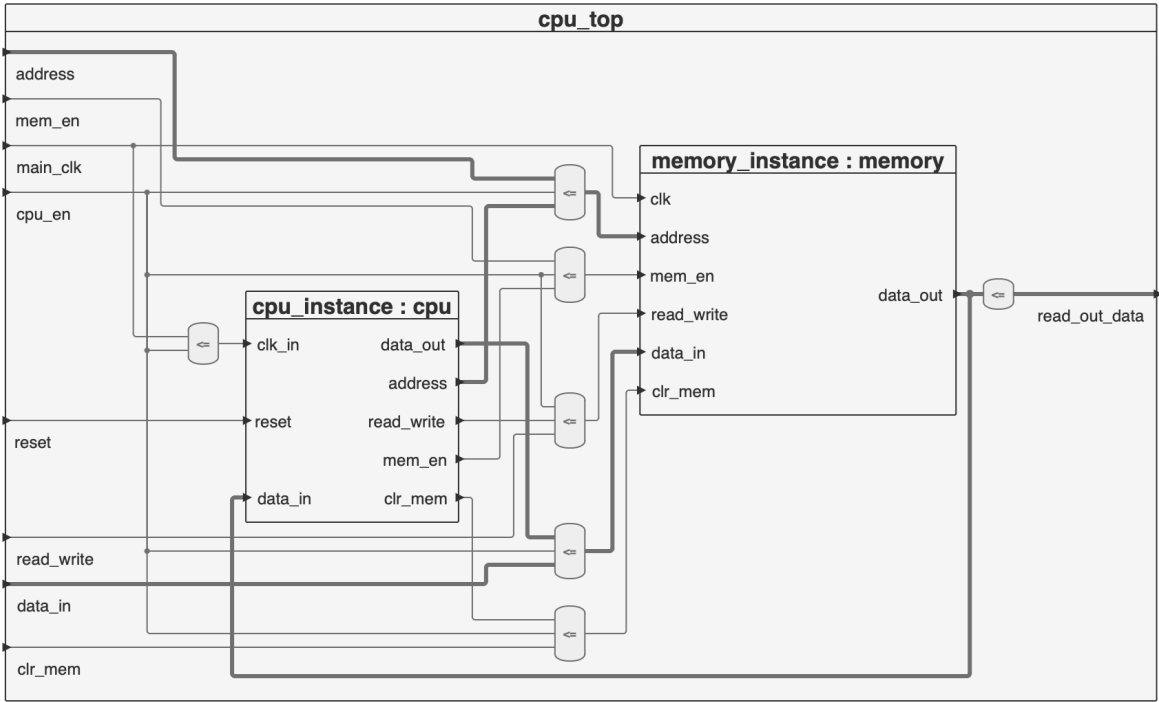

CPU: Top Level Block

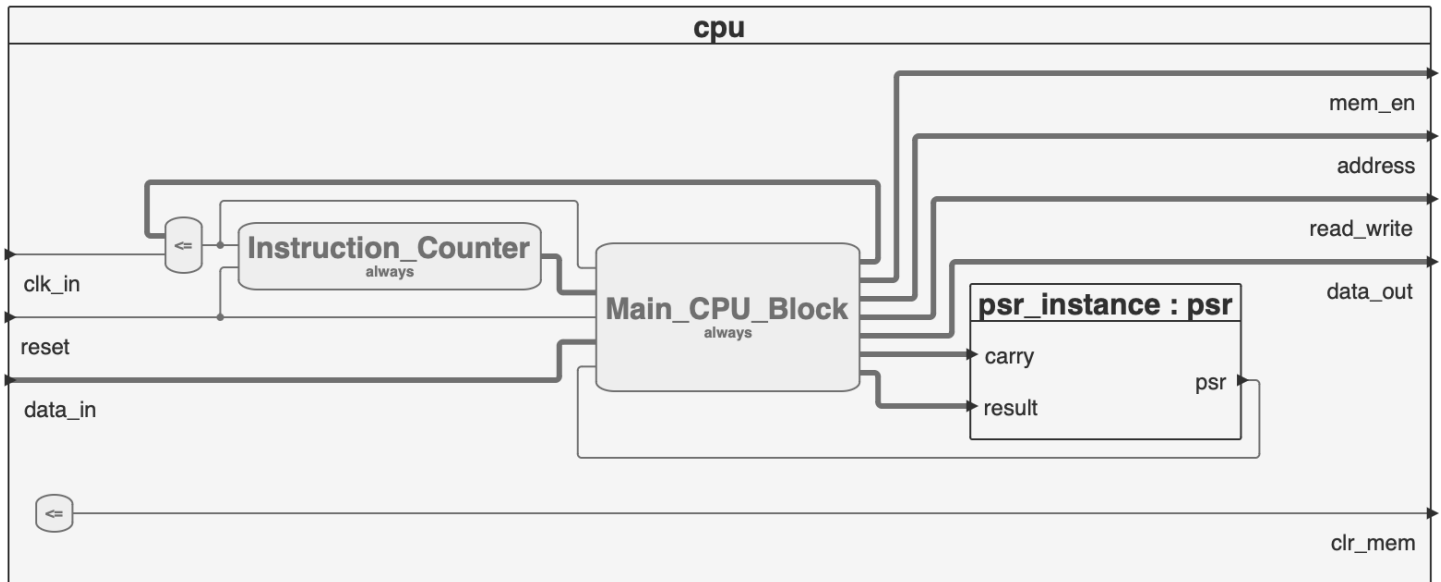

CPU: CPU Block

```
# -----
# PROGRAMING MODE
# PROGRAMING N=6 TEST PROGRAM...
#   INST, SRC, DEST
#   -> LD MEM0 REG3
#   -> CMP REG3 REG4
#   -> STR REG4 MEM1
# RUNNING N=6 TEST PROGRAM...
# *****
# CHECKIG MEMORY VALUE AT LOCATION 1
# EXPECTED VALUE OF -6 (2s comp of 6)
# read_out_data in hex: ffffffff
# read_out_data in dec:      -6
# -----
```

CPU: N Complement Program Testbench

Assembly Program is commented in TB above

Successful result of program is stored back in MEM and read as output of TB

Lab Part 3_ OnesCounterCPU_Program:

```
# -----
# PROGRAMING MODE
# PROGRAMING NUMBER OF ONES TEST PROGRAM...
#
# VALUES IN MEM:
# hX000 -> test_number
# hX001 -> 0
#
# PROGRAM:
# ADRS -> INST, SRC, DEST
# hX004 -> LD MEM0 REG0
# hX005 -> LD MEM1 REG2
# hX006 -> SHF Left1 REG0
# hX007 -> BRANCH NO CARRY ADRS_11
# hX008 -> ADD IMED_1 REG2
# hX009 -> ADD IMED_0 REG0
# hX00a -> BRANCH ZERO ADRS_12
# hX00b -> BRANCH ALWAYS ADRS_6
# hX00c -> STR REG2 MEM1
# hX00d -> HLT
# RUNNING NUMBER OF ONES TEST PROGRAM...
# *****
# CHECKING MEMORY VALUE AT LOCATION 1, WHERE RESULT IS STORED
# NUMBER OF 1's IN 10101010101010100001000100010001
# *****
# read_out_data in bin: 00000000000000000000000000001100
# read_out_data in hex: 0000000c
# read_out_data in dec:          12
# -----
```

CPU: Ones Counter Program Testbench

Assembly Program is commented in TB above

Successful result of program is stored back in MEM and read as output of TB

Lab Part 4_ MultiplierCPU_Program:

```
# -----
# PROGRAMING MODE
# PROGRAMING MULTIPLICATION TEST PROGRAM...
#
# VALUES IN MEM:
# hX000 -> A VALUE = 0000000e
# hX001 -> B VALUE = 0000000f
# hX002 -> C INITIAL = 00000000
# hX00f -> DECREMENT = ffffffff
#
# ADRS -> INST SRC DEST
# hX004 -> LD MEM0 REG0
# hX005 -> LD MEM1 REG1
# hX006 -> LD MEM2 REG2
# hX007 -> LD MEMf REGf
# hX008 -> ADD REG0 REG2
# hX009 -> ADD REGf REG1
# hX00a -> BRA ZERO ADRS00c
# hX00b -> BRA POS ADRS008
# hX00c -> STR REG2 MEM2
# hX00d -> HLT
# RUNNING MULTIPLICATION TEST PROGRAM...
# *****
# CHECKING MEMORY VALUE AT LOCATION F3
# MULTIPLIED 14 * 15, EXP RES: 210
# read_out_data in bin: 000000000000000000000000011010010
# read_out_data in hex: 000000d2
# read_out_data in dec: 210
# -----
```

CPU: Multiplication Program Testbench

Assembly Program is commented in TB above

Successful result of program is stored back in MEM and read as output of TB