

# **ECSE 318 Lab 4 Report**

## **Group 5**

Nabeeh Daouk and Kyle Heston

Thursday, November 2, 2023


## Problem 1

```
run -all
Testing Multiplication Functionality for 2*6 Below:
Multiplicand: 0010 * Multiplier:0110 = Product:00001100
Multiplicand: 2 * Multiplier: 6 = Product: 12

Testing Multiplication Functionality for 12*3 Below:
Multiplicand: 1100 * Multiplier:0011 = Product:00100100
Multiplicand: 12 * Multiplier: 3 = Product: 36


ACTIVATING DASHED PATH, Question 1c:
Testing Multiplication Functionality for 12*3 Below:
Multiplicand: 1101 * Multiplier:1101 = Product:10101001
Multiplicand: 13 * Multiplier:13 = Product:169
```
 
### Parallel Multiplier Testbench Results



**Critical Path Input:** input sequence of  $x=1101$  and  $y=1101$  activates the critical path

## Problem 2

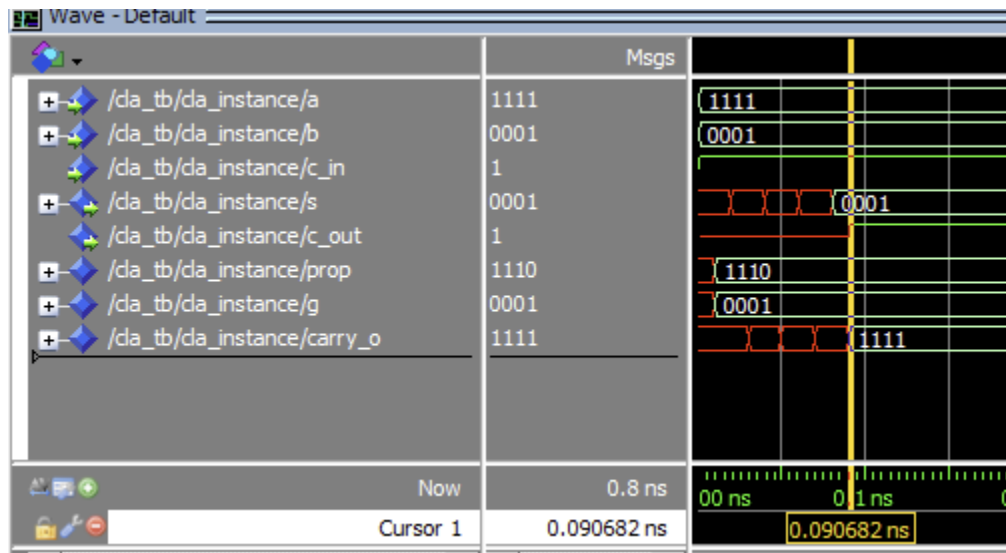

#10 delay in ps; 0.907 ns = ~90ps; **9 Gate Delay to c\_out, 8 to sum**

```

LONGEST PROPAGATION DELAY:
A: 1111 + B:0001 (c_in=1) = Sum:0001 (c_out=1)
A: 15 + B: 1 (c_in=1) = Sum: 1 (c_out=1)

Testing Addition Functionality:
A: 0101 + B:0111 (c_in=0) = Sum:1100 (c_out=0)
A: 5 + B: 7 (c_in=0) = Sum:12 (c_out=0)

Testing Addition Functionality:
A: 0100 + B:0011 (c_in=1) = Sum:1000 (c_out=0)
A: 4 + B: 3 (c_in=1) = Sum: 8 (c_out=0)


Testing Addition Functionality:
A: 1001 + B:0101 (c_in=1) = Sum:1111 (c_out=0)
A: 9 + B: 5 (c_in=1) = Sum:15 (c_out=0)
quit -f

```

## CLA Testbench Results

### Problem 3

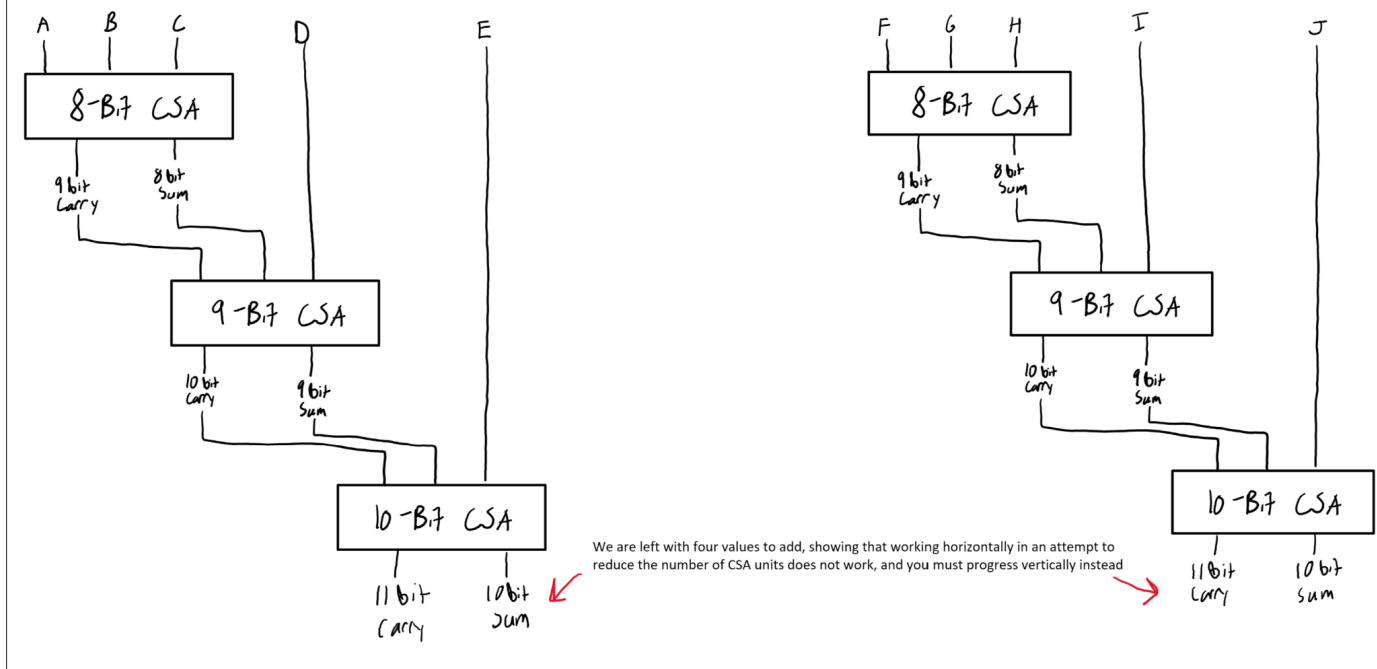A) Eight CSA stages are needed. The first CSA stage takes three inputs,  $10-3=7$ , we need 7 additional stages to take in all the inputs. An example of trying to use less than 8 CSA units is shown here:



**We cannot simplify the four values using a full adder, which takes three inputs.  
8 Total stages are used in VHDL design**

Test addition problem 1:

A: 00001011 + B:00000010 + C:00001101 + D:00000100 + E:00000101 + F:00000110 + G:00000111 + H:00001000 + I:00001001 + J:00001010 = Sum:00000000001001011

A: 11 + B: 2 + C: 13 + D: 4 + E: 5 + F: 6 + G: 7 + H: 8 + I: 9 + J: 10 = Sum: 75

Test addition problem 2:

A: 00000011 + B:00001110 + C:00000101 + D:00000110 + E:00000111 + F:00001000 + G:00010011 + H:00001010 + I:00000000 + J:00000000 = Sum:00000000001001000

A: 3 + B: 14 + C: 5 + D: 6 + E: 7 + F: 8 + G: 19 + H: 10 + I: 0 + J: 0 = Sum: 72

Test additional example:

A: 00011110 + B:00010110 + C:00010011 + D:01111110 + E:00000101 + F:01011100 + G:01000101 + H:00101100 + I:00000001 + J:00001010 = Sum:000000000110100010

A: 30 + B: 22 + C: 19 + D:126 + E: 5 + F: 92 + G: 69 + H: 44 + I: 1 + J: 10 = Sum: 418

Test additional example:

A: 11111111 + B:11111111 + C:11111111 + D:11111111 + E:11111111 + F:11111111 + G:11111111 + H:11111111 + I:11111111 + J:11111110 = Sum:000000100111110101

A: 255 + B:255 + C:255 + D:255 + E:255 + F:255 + G:255 + H:255 + I:255 + J:254 = Sum: 2549

quit -f

End time: 00:09:58 on Nov 10,2023, Elapsed time: 0:00:01

### CSA Testbench Results

## Problem 4

```

run -all
-----
Testing 7+3:

Binary Result: 000001010
Decimal Result:  10
-----

Testing 6+4:



















  






 
Binary Result: 000001010
Decimal Result:  10
-----

Testing 94+27:

Binary Result: 001111001
Decimal Result: 121
-----

```

### Bit-Serial Adder Testbench Results

 /bit_ser_add_tb/bit_ser_add_instance/dk	1	
 /bit_ser_add_tb/bit_ser_add_instance/A	1	
 /bit_ser_add_tb/bit_ser_add_instance/B	1	
 /bit_ser_add_tb/bit_ser_add_instance/dr_n	1	
 /bit_ser_add_tb/bit_ser_add_instance/set_n	1	
  /bit_ser_add_tb/bit_ser_add_instance/result	000000000	
 /bit_ser_add_tb/bit_ser_add_instance/serial_result	0	
 /bit_ser_add_tb/bit_ser_add_instance/carry_reg	0	
  /bit_ser_add_tb/bit_ser_add_instance/addend	11000000	
  /bit_ser_add_tb/bit_ser_add_instance/augand	10000000	
  /bit_ser_add_tb/bit_ser_add_instance/result_internal	000000000	

**Added an output port 'serial\_result' to give 'result' value in a serial format instead of a singular 8 bit parallel output. Result of first problem shown above (LSB to MSB)**


## Problem 5

```
loading work.divider (behavioral)
Loading work.bitsubtractor (behavioral)
Loading work.fullsubtractor (behavioral)
run -all
Testing Division Functionality for 6/2 Below:
Dividend: 0110 / Divisor: 0010 = Quotient: 0011 and Remainder: 0000
Dividend: 6 / Divisor: 2 = Quotient: 3 and Remainder: 0


Testing Division Functionality for 7/2 Below:
Dividend: 0111 / Divisor: 0010 = Quotient: 0011 and Remainder: 1
Dividend: 7 / Divisor: 2 = Quotient: 3 and Remainder: 1
** Note: $stop : C:/Users/nabeehdaouk/source/repos/ECSE318/Lab4/Part5/divider_tb.v(31)
```
 
### Booth Divider Testbench Results

Created a parallel divider using an ARRAY of subtractor instances as drawn below--x is dividend, y is divisor. Array is described in VHDL.



## Problem 6

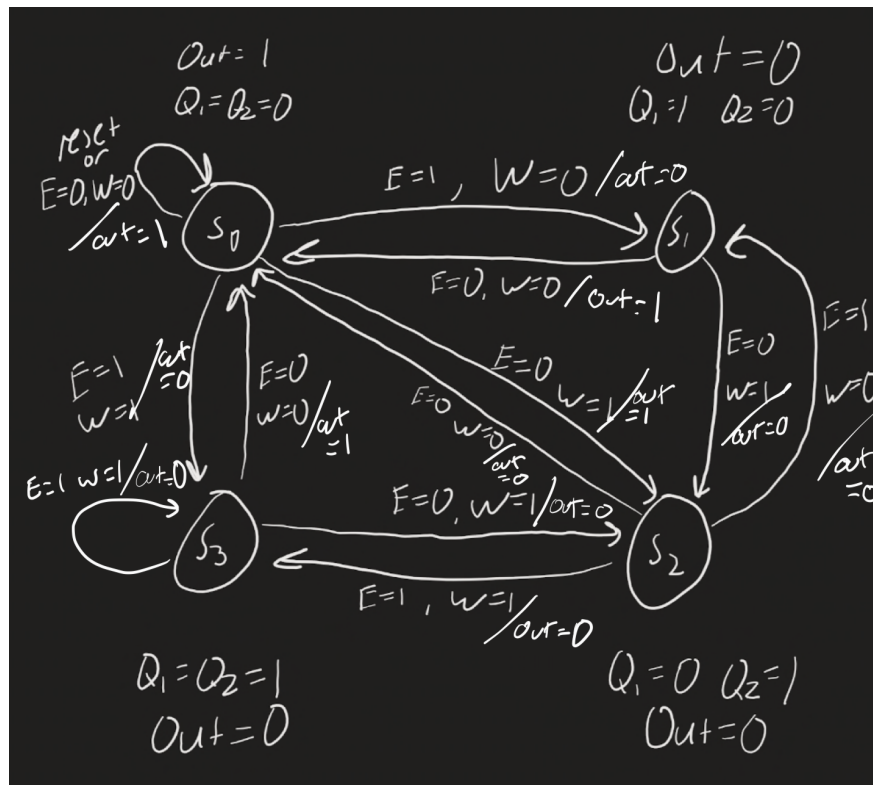

## Problem 6 State Diagram

```

# Loading work.prob_six_struct(behavioral)
# Loading work.prob_six_behav(behavioral)
# run -all
# NOTE: This is a Moore Machine, so we expect output to reflect the state
#       Output is only expected to be asserted when we are in S0
# STATE=q2q1
#
# Start in S0::
# E: 0      W:0      BEHAVIORAL_OUT:1      STRUCTURAL_OUT:1
#
# Transition to S1
# E: 1      W:0      BEHAVIORAL_OUT:0      STRUCTURAL_OUT:0
#
# Transition to S2
# E: 1      W:1      BEHAVIORAL_OUT:0      STRUCTURAL_OUT:0
#
# Transition to S3
# E: 0      W:1      BEHAVIORAL_OUT:0      STRUCTURAL_OUT:0
#
# Transition Back to S0
# E: 0      W:0      BEHAVIORAL_OUT:1      STRUCTURAL_OUT:1
#
# ** Note: $stop      : C:/Users/nabeehdaouk/source/repos/ECSE318/Lab4/Part6/prob_six_tb.v(68)
#       Time: 500 ps  Iteration: 0  Instance: /prob_six_tb
# Break in Module prob_six_tb at C:/Users/nabeehdaouk/source/repos/ECSE318/Lab4/Part6/prob_six_tb.v line 68
# Stopped at C:/Users/nabeehdaouk/source/repos/ECSE318/Lab4/Part6/prob_six_tb.v line 68
  
```

## Problem 6 Testbench Results

B) The state diagram drawn shows what Out equals based on input E and W. The VHDL models show the same input/output combinations as the drawn diagram. Follows expected state transitions and outputs (seen in plots (state value registers highlighted above in waveform). We can see that the structural and behavioral implementations have the same states.

D) Both behavioral and structural models have the same testbench output.

