

ECSE 318 Lab 1 Report

Group 5

Nabeeh Daouk and Kyle Heston

Tuesday, September 24, 2023

Problem 1

Testing Multiplication Functionality for 2×6 Below:

Multiplicand: 0010 * Multiplier: 0110 = Product: 00001100

Multiplicand: 2 * Multiplier: 6 = Product: 12

Testing Multiplication Functionality for 12×3 Below:

Multiplicand: 1100 * Multiplier: 0011 = Product: 00100100

Multiplicand: 12 * Multiplier: 3 = Product: 36


ACTIVATING DASHED PATH, Question 1c:

Testing Multiplication Functionality for 12×3 Below:

Multiplicand: 1101 * Multiplier: 1101 = Product: 10101001


Multiplicand: 13 * Multiplier: 13 = Product: 169

Problem 1 Testbench Results

 

Critical Path Input: input sequence of $x=1101$ and $y=1101$ activates the critical path

Problem 2

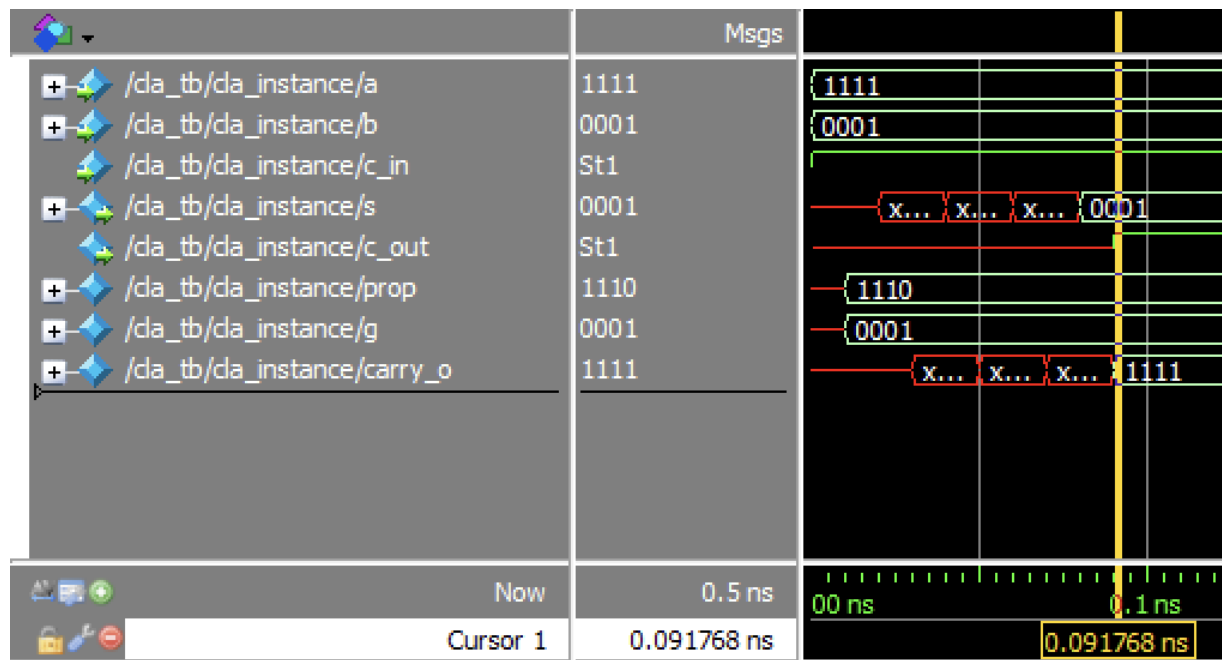

#10 delay in ps; 0.91 ns = ~90ps; 9 Gate Delay to c_out, 8 to sum

LONGEST PROPIGATION DELAY:

A: 1111 + B:0001 (c_in=1) = Sum:0001 (c_out=1)

A: 15 + B: 1 (c_in=1) = Sum: 1 (c_out=1)

Testing Addition Functionality:

A: 0101 + B:0111 (c_in=0) = Sum:1100 (c_out=0)

A: 5 + B: 7 (c_in=0) = Sum:12 (c_out=0)

Testing Addition Functionality:

A: 0100 + B:0011 (c_in=1) = Sum:1000 (c_out=0)

A: 4 + B: 3 (c_in=1) = Sum: 8 (c_out=0)

Testing Addition Functionality:


A: 1001 + B:0101 (c_in=1) = Sum:1111 (c_out=0)

A: 9 + B: 5 (c_in=1) = Sum:15 (c_out=0)

Problem 2 Testbench Results

Problem 3

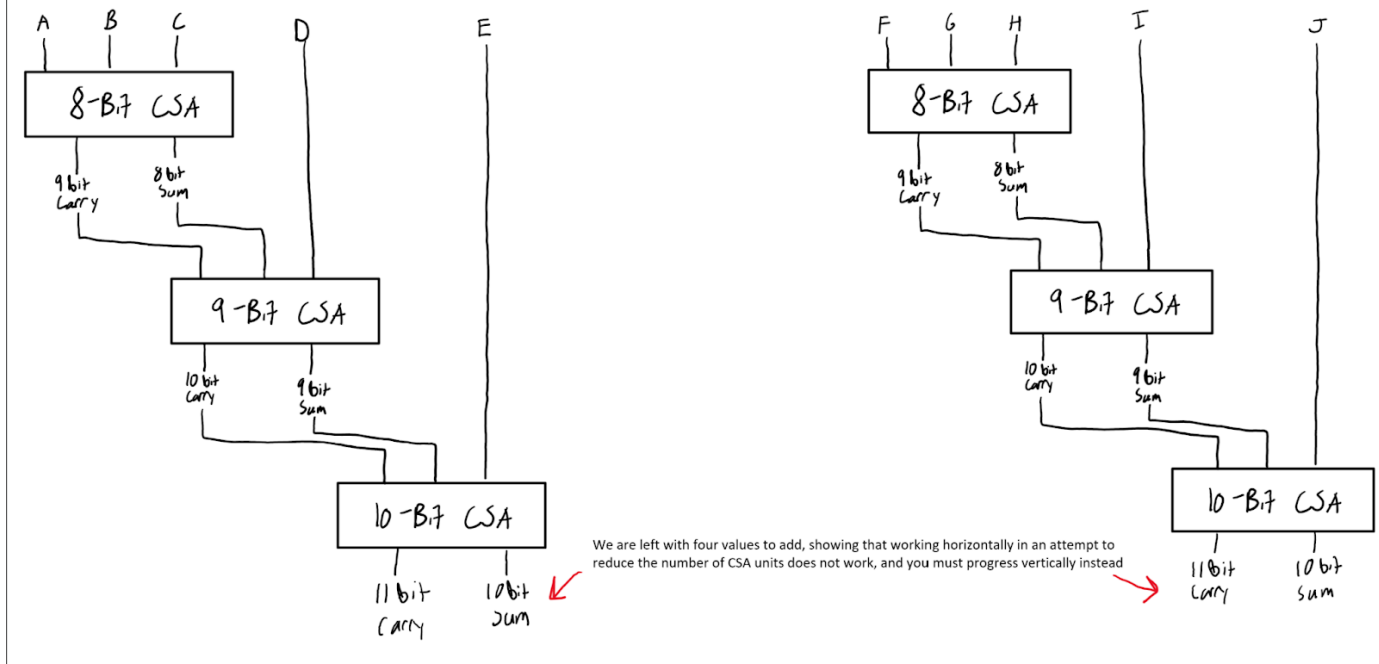A) Eight CSA stages are needed. The first CSA stage takes three inputs, $10-3=7$, we need 7 additional stages to take in all the inputs. An example of trying to use less than 8 CSA units is shown here:




**We cannot simplify the four values using a full adder, which takes three inputs.
8 Total stages are used in Verilog design**

```
# run -all
# Test addition problem 1:
# A: 00001011 + B:00000010 + C:00001101 + D:00000100 + E:00000101 + F:00000110 + G:00000111 + H:00001000 + I:00001001 + J:00001010 = Sum:000000000001001011
# A: 11 + B: 2 + C: 13 + D: 4 + E: 5 + F: 6 + G: 7 + H: 8 + I: 9 + J: 10 = Sum: 75
#
# Test addition problem 2:
# A: 00000011 + B:00001110 + C:00000101 + D:00000110 + E:00000111 + F:00001000 + G:00010011 + H:00001010 + I:00000000 + J:00000000 = Sum:000000000001001000
# A: 3 + B: 14 + C: 5 + D: 6 + E: 7 + F: 8 + G: 19 + H: 10 + I: 0 + J: 0 = Sum: 72
#
# Test additional example:
# A: 00011110 + B:00010110 + C:00010011 + D:01111110 + E:00000101 + F:01011100 + G:01000101 + H:00101100 + I:00000001 + J:00001010 = Sum:000000000110100010
# A: 30 + B: 22 + C: 19 + D:126 + E: 5 + F: 92 + G: 69 + H: 44 + I: 1 + J: 10 = Sum: 418
#
# Test additional example:
# A: 11111111 + B:11111111 + C:11111111 + D:11111111 + E:11111111 + F:11111111 + G:11111111 + H:11111111 + I:11111111 + J:11111110 = Sum:000000100111110101
# A: 255 + B:255 + C:255 + D:255 + E:255 + F:255 + G:255 + H:255 + I:255 + J:254 = Sum: 2549
# quit -f
# End time: 23:02:27 on Sep 22,2023, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
```

Activate Windows

Problem 3 Testbench Results

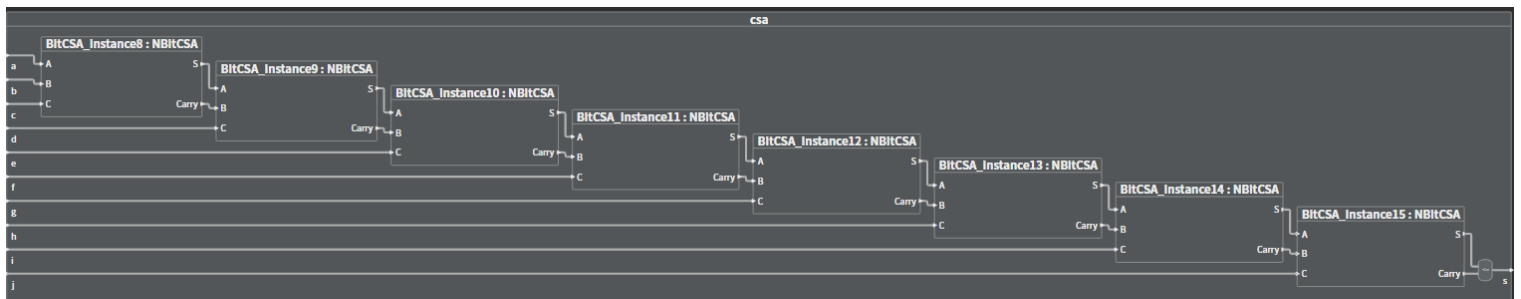

Problem 3 CSA BBlock Diagram

Problem 4

```
# Test multiplication problem 1:
# Multiplicand: 10110 * Multiplier:00100 = Product:1111011000
# Multiplicand: -10 * Multiplier: 4 = Product: -40
#
# Test multiplication problem 2:
# Multiplicand: 01011 * Multiplier:11101 = Product:1111011111
# Multiplicand: 11 * Multiplier: -3 = Product: -33
#
# Test multiplication problem 3:
# Multiplicand: 10110 * Multiplier:10101 = Product:0001101110
# Multiplicand: -10 * Multiplier: -11 = Product: 110
```


Problem 4 Testbench Results

Problem 5


```
# Testing Division Functionality for 6/2 Below:
# Dividend: 0110 * Divisor: 0010 = Quotient:0011 and Remainder: 0000
# Dividend: 6 * Divisor: 2 = Quotient: 3 and Remainder: 0
#
# Testing Division Functionality for 7/2 Below:
# Dividend: 0111 * Divisor: 0010 = Quotient: 0011 and Remainder: 1
# Dividend: 7 * Divisor: 2 = Quotient: 3 and Remainder: 1
# quit -f
# End time: 01:14:26 on Sep 22,2023, Elapsed time: 0:00:00
# Errors: 0, Warnings: 0
```

Problem 5 Testbench Results

Created a parallel divider using an ARRAY of subtractor instances as drawn below--x is dividend, y is divisor. Array is described in Verilog.

 

Problem 6

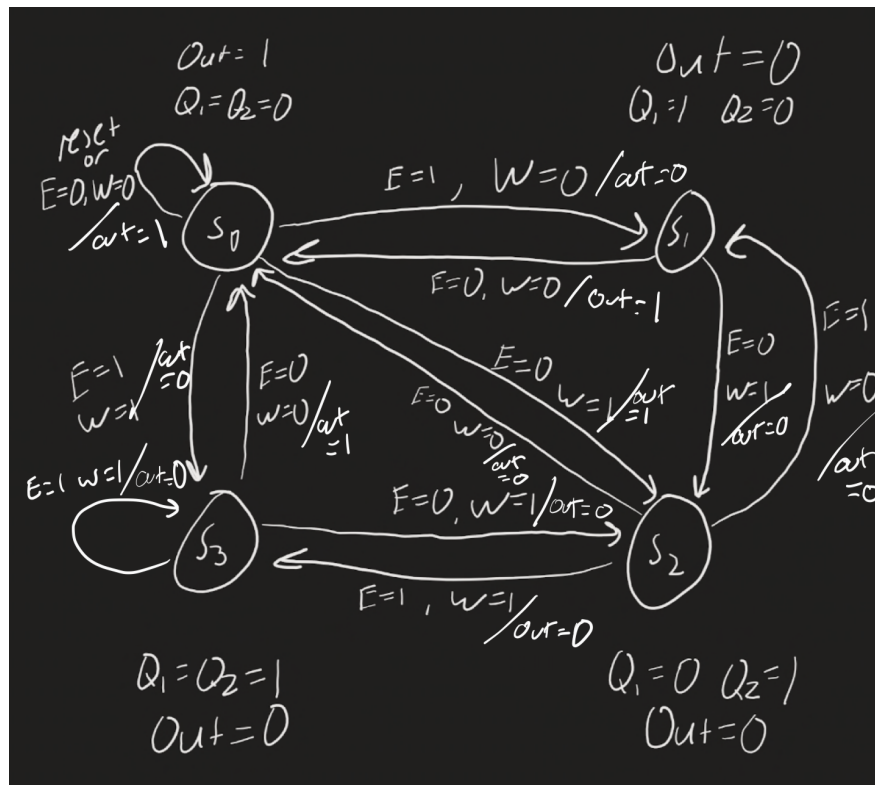

Problem 6 State Diagram

```

STATE=q2q1
Start in S0:
E: 0    W:0    BEHAVIORAL_OUT:1    STRUCTURAL_OUT:1


Transition to S1
E: 1    W:0    BEHAVIORAL_OUT:0    STRUCTURAL_OUT:0

Transition to S2
E: 1    W:1    BEHAVIORAL_OUT:0    STRUCTURAL_OUT:0

Transition to S3
E: 0    W:1    BEHAVIORAL_OUT:0    STRUCTURAL_OUT:0

Transition Back to S0
E: 0    W:0    BEHAVIORAL_OUT:1    STRUCTURAL_OUT:1

```

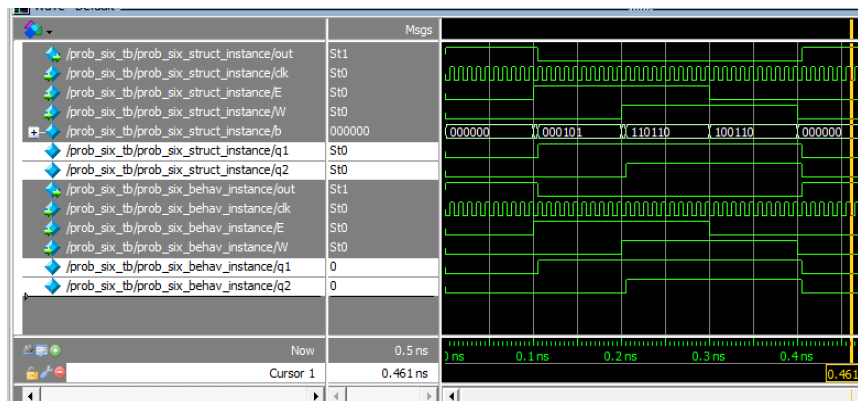

Problem 6 Testbench Results

- B) The state diagram drawn shows what Out equals based on input E and W. The Verilog models show the same input/output combinations as the drawn diagram. Follows expected state transitions and outputs (seen in plots (state value registers highlighted above in waveform). We can see that the structural and behavioral implementations have the same states.
- D) Both behavioral and structural models have the same testbench output.